

NAME: Servet Çelik




STUDENT ID: 21947071

8 BIT MULTIPLIER & 8 BIT ALU PROJECT**1) INTRODUCTION:**

In this project, an 8-bit multiplier and an 8-bit ALU is designed. According to article of Akshata R., Prof. V.P. Gejji, Prof. B.R. Pandurangi called "ANALYSIS OF VEDIC MULTIPLIER", Vedic multipliers have simpler architecture and smaller path delay than array multipliers. That's why Vedic multiplier architecture is preferred for the 8-bit multiplier. The ALU is designed in this project handles 8 different operations. These operations are 8-bit addition, 8-bit subtraction, 4-bit multiplication, 8-bit inversion, 8-bit one digit left shift, 8-bit one-digit right shift, 8-bit two digits right shift and 8-bit buffer. The 8-bit multiplier gets two 8-bit numbers as input and gives 16-bit output, but the multiplexer in the 8-bit ALU gets an 8-bit input. So, 4-bit multiplier is implemented instead of 8-bit multiplier in the ALU.


2) TRANSISTOR LEVEL DESIGN:

Icons of each type of conventional gates were created by using NMOSs and PMOSs with proper sizing.

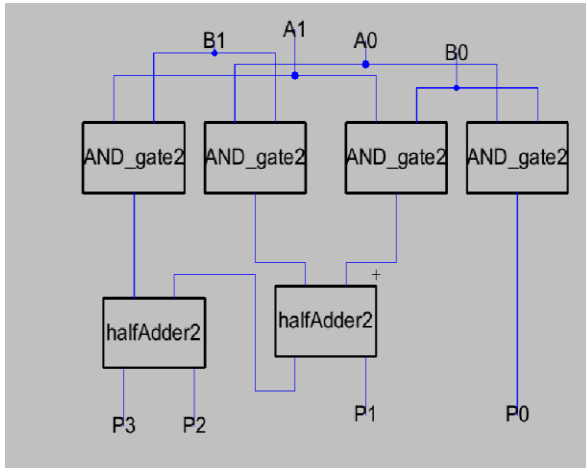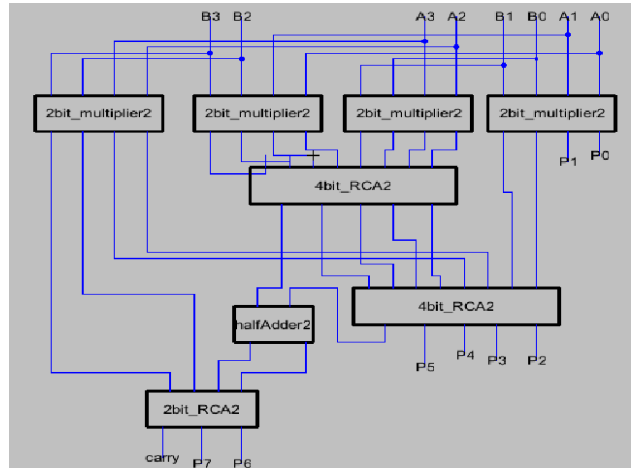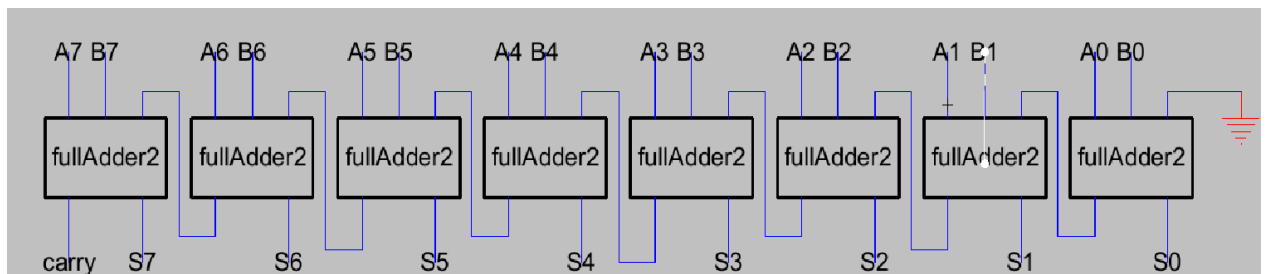
2-bit Multiplier:**4-bit Multiplier:****8-bit Ripple Carry Adder (RCA):**

The 2-bit RCA and 4-bit RCA are not shown since they have similar architecture with 8-bit RCA.


8-bit multiplier:

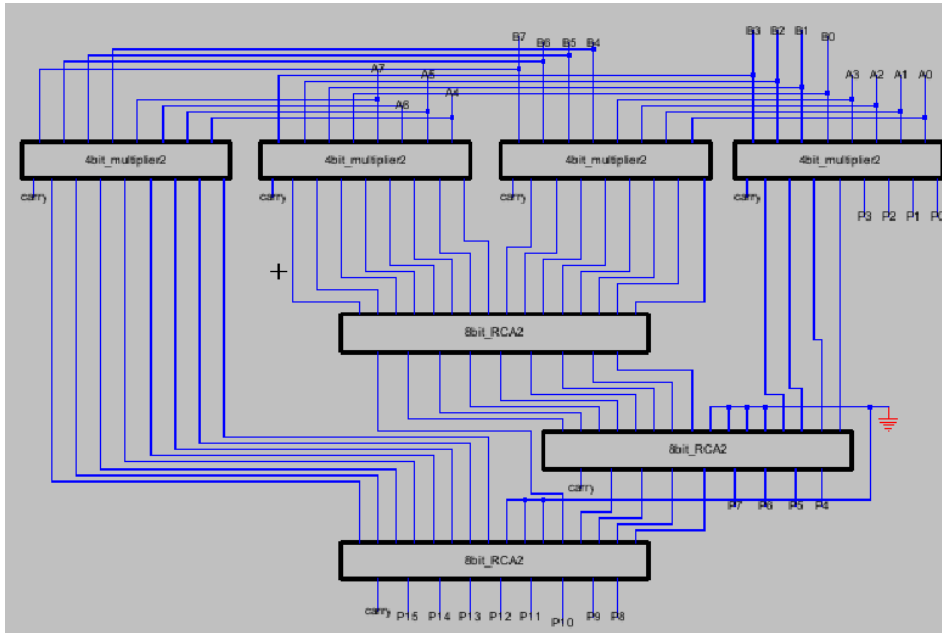


4x1 MUX:

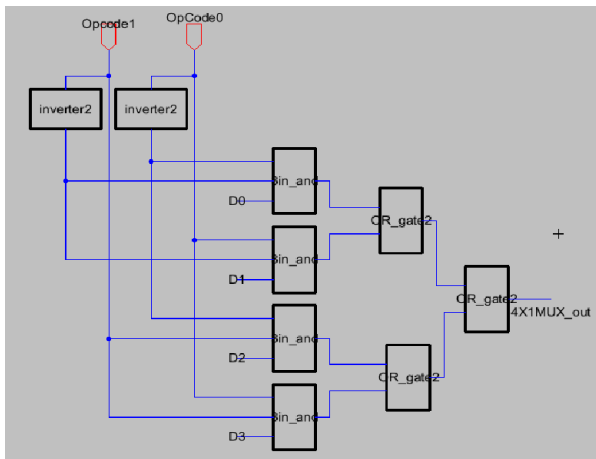

8x1 MUX:

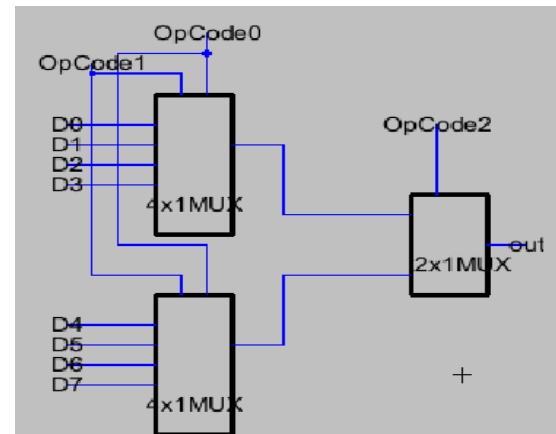


8-bit Shifter:

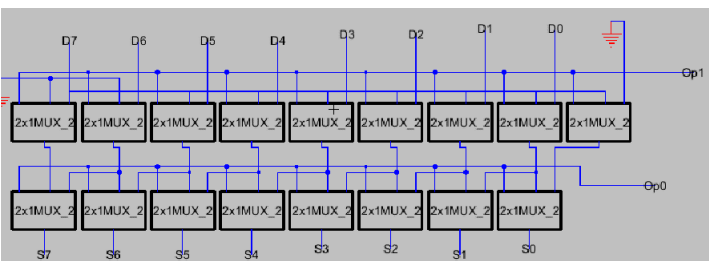

This shifter was designed by using 2x1 MUXs. The mode of shifting is determined by Op1 and Op0.


Op1	Op0	Function
0	0	1 bit left
0	1	buffer
1	0	1 bit right
1	1	2 bits right

8-bit Adder & Subtractor:

 

This 8-bit adder & subtractor was designed by using fulladders and XOR gates. It makes subtraction ($A-B$) when sub2, sub1 and sub0 are high, otherwise it makes an addition operation ($A+B$). Sub2, sub1 and sub0 are determined by the OpCodes in the ALU.

8-bit ALU:

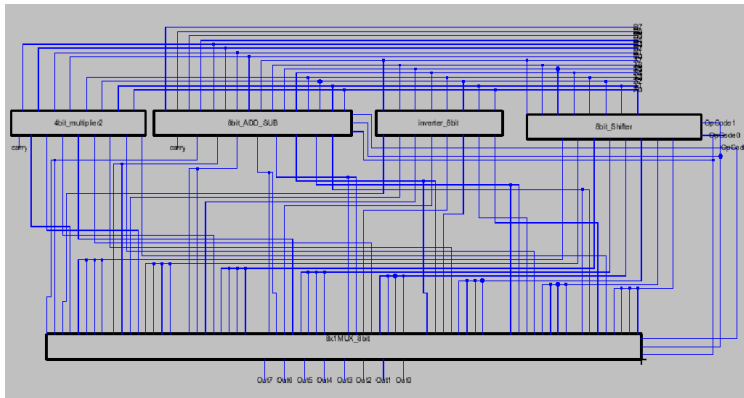


Function table of 8-bit ALU


OpCode2	OpCode1	OpCode0	Function
0	0	0	1 left ($A \ll 1$)
0	0	1	Buffer (A)
0	1	0	1 right ($A \gg 1$)
0	1	1	2 right ($A \gg 2$)
1	0	0	Multiplier ($A * B$)
1	0	1	Inverter ($\sim A$)
1	1	0	Add ($A+B$)
1	1	1	Subtraction ($A-B$)

3) LAYOUT DESIGN:


2-bit Multiplier:

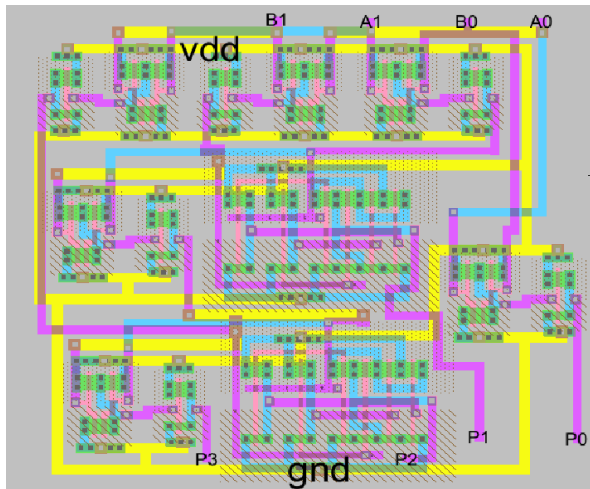


4-bit Multiplier:

 

8-bit Ripple Carry Adder:

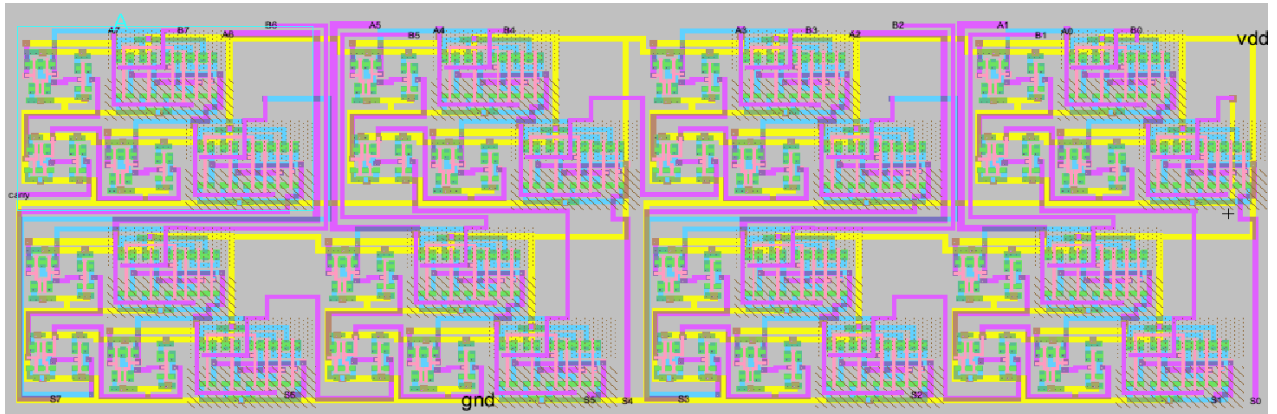


8-bit multiplier:

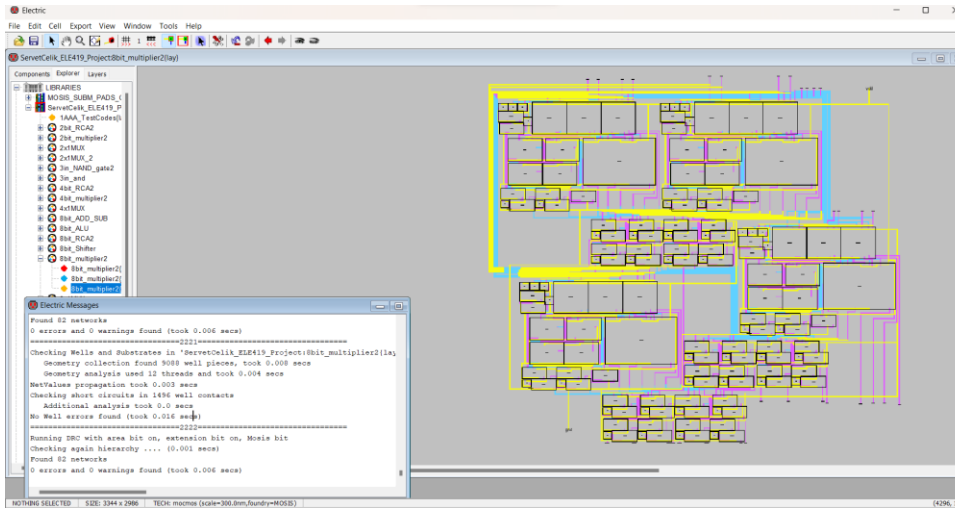


This 8-bit multiplier is created by using four 4-bit multipliers and three 8-bit RCAs. In the picture, I could not go down to transistor level because of my computer quality. It shows just green blocks when I go down to first level.

Pin connections of 8-bit multiplier:

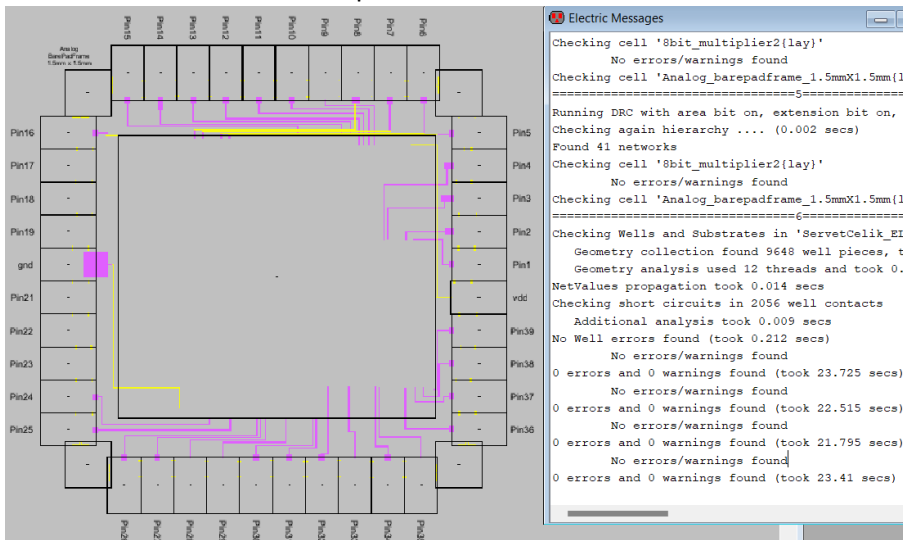


vdd	vdd	gnd	gnd
A7	Pin8	Out15	Pin24
A6	Pin7	Out14	Pin25
A5	Pin6	Out13	Pin26
A4	Pin5	Out12	Pin27
A3	Pin4	Out11	Pin28
A2	Pin3	Out10	Pin29
A1	Pin2	Out9	Pin30
A0	Pin1	Out8	Pin31
B7	Pin16	Out7	Pin32
B6	Pin15	Out6	Pin33
B5	Pin14	Out5	Pin34
B4	Pin13	Out4	Pin35
B3	Pin12	Out3	Pin36
B2	Pin11	Out2	Pin37
B1	Pin10	Out1	Pin38
B0	Pin9	Out0	Pin39


8-bit Shifter:

 


4x1 MUX:

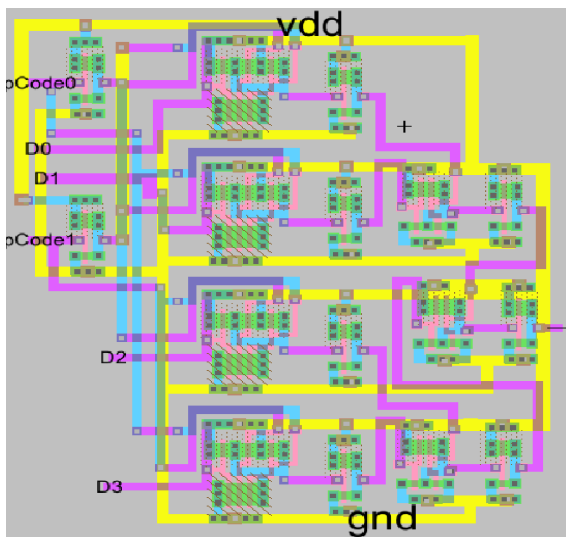


8x1 MUX:

 

8-bit Adder & Subtractor:

 

8-bit ALU:

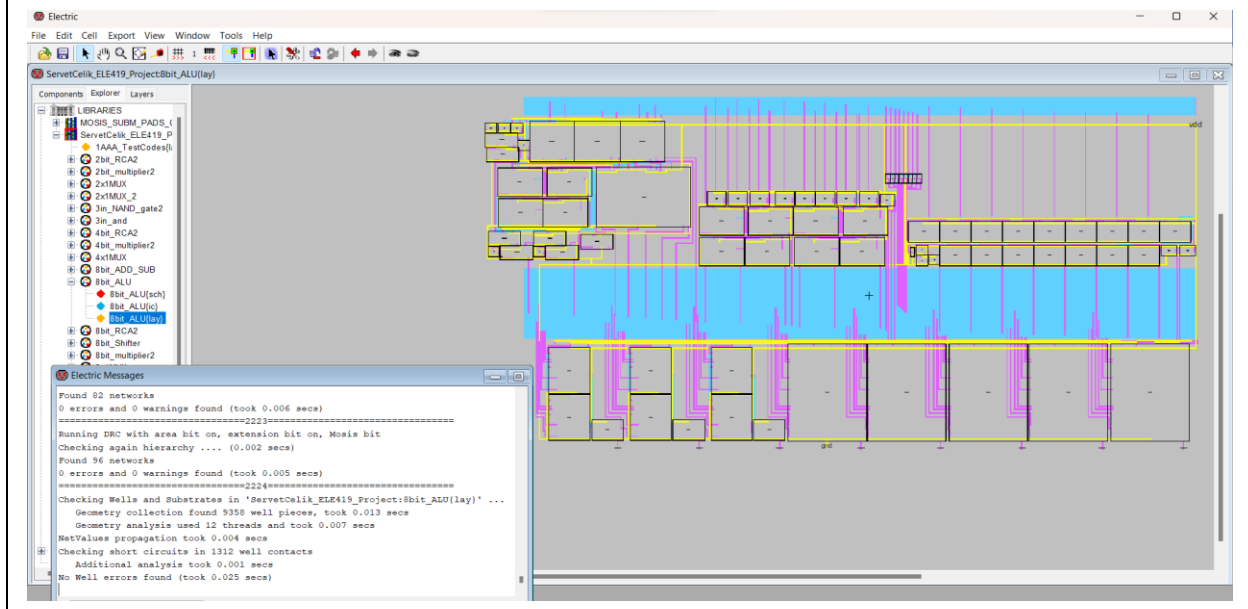


4) SIMULATION RESULTS:

- In the simulation part, the outputs are separated as 1s and 0s to have a better visualization.

a. Multiplication:

 i. A=00001111, B=10101010

```
vdd vdd 0 DC 5
VinA7 A7 0 DC 0
VinA6 A6 0 DC 0
VinA5 A5 0 DC 0
VinA4 A4 0 DC 0
VinA3 A3 0 DC 5
VinA2 A2 0 DC 5
VinA1 A1 0 DC 5
VinA0 A0 0 DC 5
VinB7 B7 0 DC 5
VinB6 B6 0 DC 0
VinB5 B5 0 DC 5
VinB4 B4 0 DC 0
VinB3 B3 0 DC 5
VinB2 B2 0 DC 0
VinB1 B1 0 DC 5
VinB0 B0 0 DC 0
.tran 10u 40u
```




The output is separated as 1s and 0s. So, the above output shows that: $A * B = 0000\ 1001\ 1111\ 0110$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	0	1	0	0	1	1	1	1	1	0	1	1	0

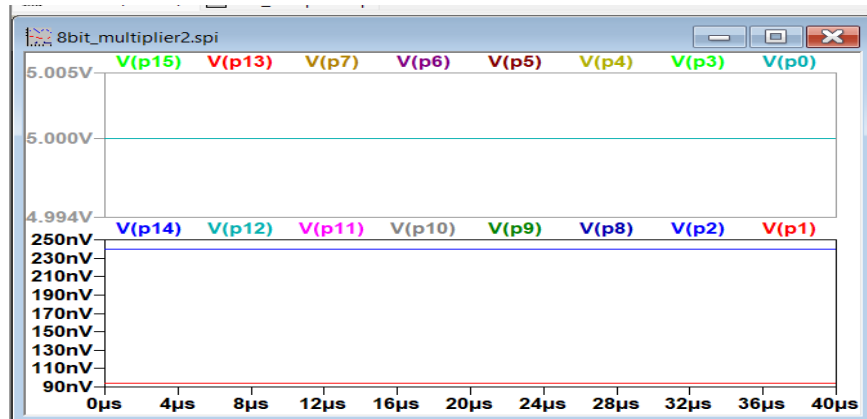ii. $A=11001011$, $B=11001011$

```
vdd vdd 0 DC 5
VinA7 A7 0 DC 5
VinA6 A6 0 DC 5
VinA5 A5 0 DC 0
VinA4 A4 0 DC 0
VinA3 A3 0 DC 5
VinA2 A2 0 DC 0
VinA1 A1 0 DC 5
VinA0 A0 0 DC 5
VinB7 B7 0 DC 5
VinB6 B6 0 DC 5
VinB5 B5 0 DC 0
VinB4 B4 0 DC 0
VinB3 B3 0 DC 5
VinB2 B2 0 DC 0
VinB1 B1 0 DC 5
VinB0 B0 0 DC 5
.tran 10u 40u
```




The output is separated as 1s and 0s. So, the above output shows that: $A * B = 1010\ 0000\ 1111\ 1001$.

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
1	0	1	0	0	0	0	0	1	1	1	1	1	0	0	1

 iii. $A=10111011$, $B=00000001$

```
vdd vdd 0 DC 5
VinA7 A7 0 DC 5
VinA6 A6 0 DC 0
VinA5 A5 0 DC 5
VinA4 A4 0 DC 5
VinA3 A3 0 DC 5
VinA2 A2 0 DC 0
VinA1 A1 0 DC 5
VinA0 A0 0 DC 5
VinB7 B7 0 DC 0
VinB6 B6 0 DC 0
VinB5 B5 0 DC 0
VinB4 B4 0 DC 0
VinB3 B3 0 DC 0
VinB2 B2 0 DC 0
VinB1 B1 0 DC 0
VinB0 B0 0 DC 5
.tran 10u 40u
```




The output is separated as 1s and 0s. So, the above output shows that: $A * B = 0000\ 1001\ 1111\ 0110$.

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	0	0	0	0	0	0	0	1	0	1	1	1	0	1	1

b. ALU:

 i. Sum of A=11001011, B=11001011 (A+B)

```
vdd vdd 0 DC 5
VinOpCode0 OpCode0 0 DC 0
VinOpCode1 OpCode1 0 DC 5
VinOpCode2 OpCode2 0 DC 5
VinA7 A7 0 DC 5
VinA6 A6 0 DC 5
VinA5 A5 0 DC 0
VinA4 A4 0 DC 0
VinA3 A3 0 DC 5
VinA2 A2 0 DC 0
VinA1 A1 0 DC 5
VinA0 A0 0 DC 5
VinB7 B7 0 DC 5
VinB6 B6 0 DC 5
VinB5 B5 0 DC 0
VinB4 B4 0 DC 0
VinB3 B3 0 DC 5
VinB2 B2 0 DC 0
VinB1 B1 0 DC 5
VinB0 B0 0 DC 5
.tran 10u 40u
```




In this spice code, OpCodes are determined by using the function table of ALU. The function code of summation is 110. This summation creates an overflow, but I could not show the overflow flag since I used an 8-bit multiplexer in the ALU. So, the output is shown as: A+B = 1001 0110 instead of A+B = 1 1001 0110.

Digits								OpCodes		
7	6	5	4	3	2	1	0	Op2	Op1	Op0
1	0	0	1	0	1	1	0	1	1	0

 ii. Subtraction of A=00001111, B=10101010 (A-B)

```
vdd vdd 0 DC 5
VinOpCode0 OpCode0 0 DC 5
VinOpCode1 OpCode1 0 DC 5
VinOpCode2 OpCode2 0 DC 5
VinA7 A7 0 DC 0
VinA6 A6 0 DC 0
VinA5 A5 0 DC 0
VinA4 A4 0 DC 0
VinA3 A3 0 DC 5
VinA2 A2 0 DC 5
VinA1 A1 0 DC 5
VinA0 A0 0 DC 5
VinB7 B7 0 DC 5
VinB6 B6 0 DC 0
VinB5 B5 0 DC 5
VinB4 B4 0 DC 0
VinB3 B3 0 DC 5
VinB2 B2 0 DC 0
VinB1 B1 0 DC 5
VinB0 B0 0 DC 0
.tran 10u 40u
```



In this spice code, OpCodes are determined by using the function table of ALU. The function code of subtraction is 111. This subtraction gives a negative output, but it is not shown in the output since sign bit wasn't used in the operations. So, the output is shown as the 2's complement of the number. So, the output is shown as : A-B = 0110 0101 instead of A-B = -1001 1011.

Output digits								OpCodes		
7	6	5	4	3	2	1	0	Op2	Op1	Op0
0	1	1	0	0	1	0	1	1	1	1

iii. 1 bit shifting of A=10010001


```
vdd vdd 0 DC 5
VinOpCode0 OpCode0 0 DC 5
VinOpCode1 OpCode1 0 DC 0
VinOpCode2 OpCode2 0 DC 0
VinA7 A7 0 DC 5
VinA6 A6 0 DC 0
VinA5 A5 0 DC 0
VinA4 A4 0 DC 5
VinA3 A3 0 DC 0
VinA2 A2 0 DC 0
VinA1 A1 0 DC 0
VinA0 A0 0 DC 5
.tran 10u 40u
```



- For all the operations above same spice code is used by changing only the Opcodes, and the opcodes are determined by using function table of the ALU. Opcodes are 000 for 1-bit left shifting, 001 for buffer, 010 1-bit right shifting and 011 for 2-bit right shifting operations.

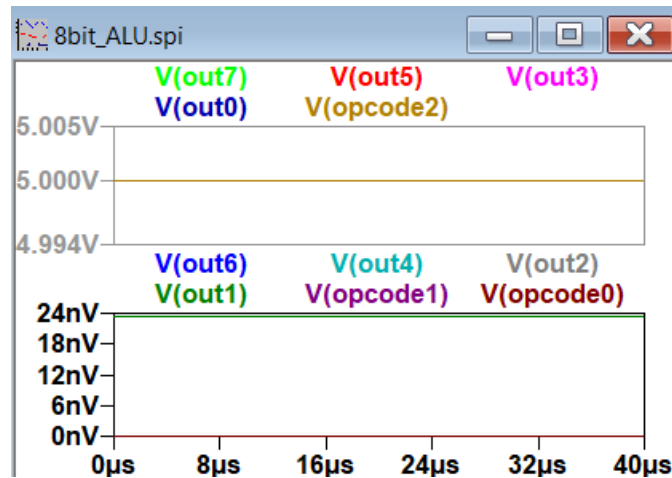iv. 4-bit multiplication of A=1101, B=1101 ($A \cdot B$)


```
vdd vdd 0 DC 5
VinOpCode0 OpCode0 0 DC 0
VinOpCode1 OpCode1 0 DC 0
VinOpCode2 OpCode2 0 DC 5
VinA3 A3 0 DC 5
VinA2 A2 0 DC 5
VinA1 A1 0 DC 0
VinA0 A0 0 DC 5
VinB3 B3 0 DC 5
VinB2 B2 0 DC 5
VinB1 B1 0 DC 0
VinB0 B0 0 DC 5
.tran 10u 40u
```



4-bit multiplier is implemented in the ALU instead of 8-bit multiplier since the output of the ALU is 8 bits. The above outputs show that: $A \cdot B = 10101001$

Output digits								OpCodes		
7	6	5	4	3	2	1	0	Op2	Op1	Op0
1	0	1	0	1	0	0	1	1	0	0

v. 8-bit inversion of A=1100 1011 (~A)

 

5) NOVELTY & PROS-CONS:

a. **Novelty:** In the multiplier part, I used Vedic multiplier architecture. Before this design, I tried array multiplier, and I saw that it was lower than this architecture. In the ALU part, I designed a shifter with 2x1 multiplexers. That design allows me to use same design for buffer, 2-bit right shifting, and 1-bit right and left shifting by just changing the OpCodes. This reduces the number of transistors and power consumption in the design.

b. Table of Pros-Cons:

Pros	Cons
High speed: this design is faster than array multiplier.	Transistor technology: An old transistor technology is used in this project.
Multiplier size: The size of multiplier design can be considered small since it fits into the frame and even leaves space.	ALU size: ALU size couldn't be reduced enough because of time constraints.
Simplicity and systematicity: This design has simple and systematic structure. So, it can be edited and developed easily by someone else.	Transistor Technology: An old transistor technology is used in the project.

c. **Functionality:** It can be implemented to a clocked system with some additional components and a proper clock distribution. The current drawn from 5V power supply is about 8.86nA. So, power consumption of the circuit can be considered low. This design is efficient in terms of power consumption and speed since the number of transistors and size of circuit is reduced to minimum level, but this efficiency can be increased if the number of transistors could be further reduced by using different kind of methodologies such as sequential logic and transmission gates.

6) REFERENCES:

[1] R. Jacob Baker, "CMOSedu.com", CMOSedu. [Online]. Available: <https://cmosedu.com/>. [Accessed: Jan 17, 2024].

[2] Akshata R., Prof. V.P. Gejji, Prof. B.R. Pandurangi, "ANALYSIS OF VEDIC MULTIPLIER", in Proceedings of the International Conference on computing, 2016